

Operational Amplifiers :-

Input and output

Parameters of op-Amp

* Differential :- it is gain with which differential gain (A_d) amplifies the difference between two input signal so it is called Differential gain

$$V_o = A_d(V_1 - V_2)$$

* Common mode Gain (A_c) :- The two input voltages which are equal in all respect to the differential amplifier ($V_1 = V_2$) for ideal case the o/p voltage

$$V_o = (V_1 - V_2) \cdot A_d = 0$$

so

$$V_c = \frac{V_1 + V_2}{2}$$

for practical differential Amplifier depends on Average Common level of two inputs and such two input signals is called common mode signal denoted as V_c .

* Common mode Rejection Ratio (CMRR) :-


The ability of a differential amplifier to reject a common mode signal is expressed by a ratio called CMRR.

* it is defined as the ratio of differential voltage gain (A_d) to common mode Gain A_c .

$$CMRR = P = \left| \frac{A_d}{A_c} \right|$$

* Input offset Voltage :- it is the differential input voltage that adjust b/w two input terminals of op-amp with out any external supply

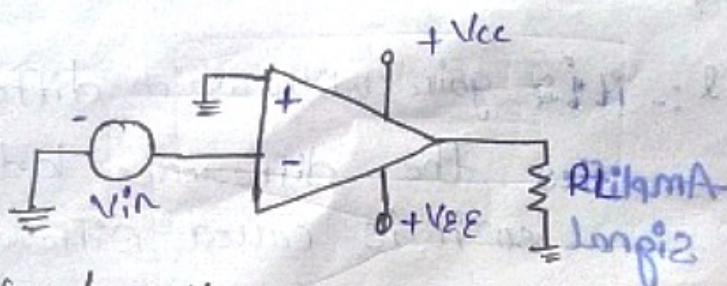
applied to make the output zero and denoted as (V_{IO})



Output offset voltage :-


It is caused due to mismatch b/w two input terminals because of collector current into two transistors are not equal and causes differential output voltage from the 1st stage and it will be buried in next stage.

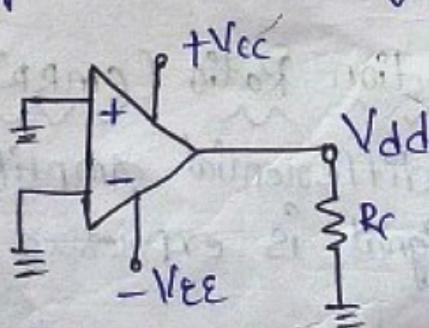* It is dc voltage either $+V_{IO}$ or $-V_{IO}$, due to potential difference b/w two input terminals to reduce V_{IO} to 0 make (V_{IO}) of proper amplification and polarity such circuit is called input off set voltage compensating Network.



Input Off set Current :-

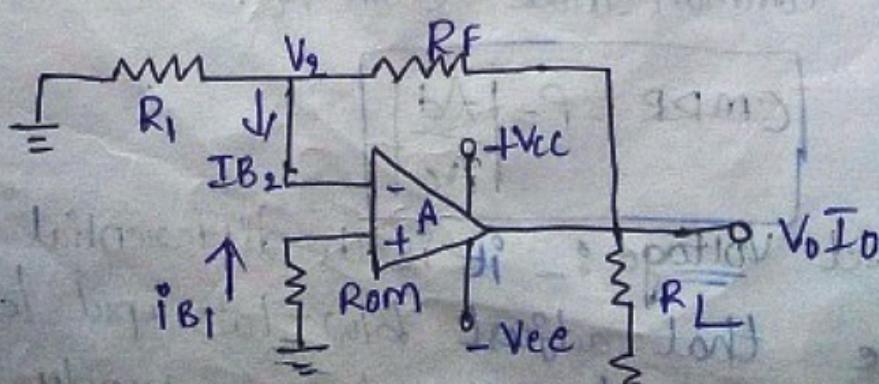The input bias current are not equal and I_{IO} is



oted as

input offset Current is used as indicator for mismatching b/w these two currents it is given by I_{IO} is modules.

$$I_{IO} = |IB_1 - IB_2|$$

V_1 and V_2 can be expressed as

$$\begin{aligned}V_1 &= R_{OM} IB_1 \\V_2 &= R_f IB_2\end{aligned}$$

$$R_{OM} = R_f = \frac{R_1 R_f}{R_1 + R_f} \quad \text{--- (1)}$$

By applying Superposition theorem, O/P off set voltage due to V_1 & V_2 in terms of IB_1 and IB_2

$$V_1 = R_{OM} IB_1$$

$$V_0 IB_2 = -R_f IB_2$$

The O/P off set voltage in terms of IB_1 & R_f ,

$$V_0 IB_2 = V_1 \left[1 + \frac{R_f}{R_1} \right] \quad \text{--- (2)}$$

where V_1 at non-inverting terminal voltage

$\left[1 + \frac{R_f}{R_1} \right]$ = Gain of non-inverting Amplifier

Sub eq (1) in eq (2) for the value of

$$V_0 I_0 = R_{OM} IB_1 \left[1 + \frac{R_f}{R_1} \right] = \frac{R_1 \times R_f}{R_1 + R_f} [IB_1] \frac{R_1 + R_f}{R_1}$$

$$V_0 I_0 + V_0 IB_2 = R_f IB_1 - R_f IB_2$$

$$= R_f (IB_1 - IB_2)$$


$$\therefore V_0 I_0 = R_f IB$$

Input bias Current :- It is defined as Average of two input bias current i_{B1} and i_{B2}

$$IB = \frac{i_{B1} + i_{B2}}{2}$$

where i_{B1} = IIP bias current flowing into non-inverting terminal.

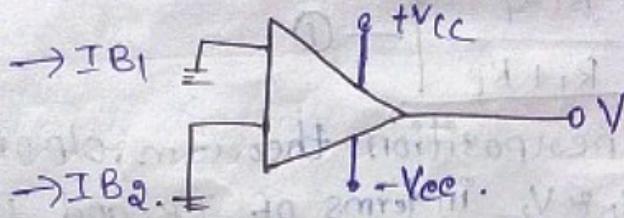
where i_{B2} = n...n...n...n inverting terminal.



for the differential Amp, the bias current is not same so, it is equal to one of the bias current.

$$IB = i_{B1} = i_{B2}$$

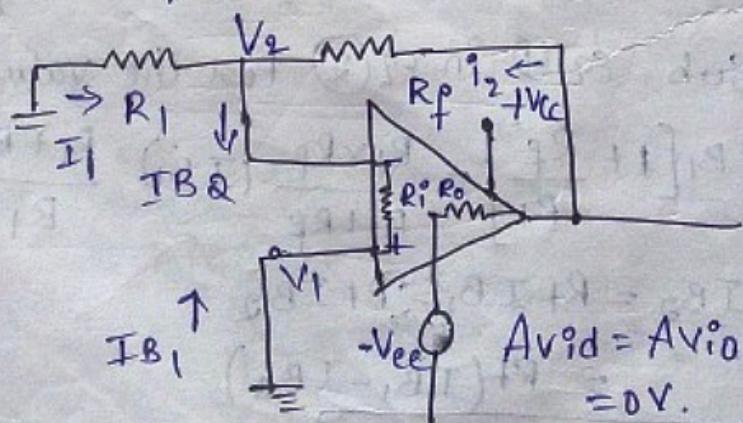for getting the off set voltage caused by the IIP bias current, IB in the inverting and non inverting Amplifiers and the device is it to eliminate or minimize it.



Non Inverting terminal is connected to ground so, $V_1 = 0V$

$Av_{io} = 0V$, $V_{io} = 0V$ the voltages at V_2

Average of

g into non-

inverting terminal.

ent is not current.

ed by the and non it to

around So,

$$V_2 = (R_i \parallel R_f) I_B 2$$

$$V_2 = \frac{R_i R_f}{R_i + R_f} \cdot I_B 2 \quad \text{--- (1)}$$

Model Equation at. V_2

$$I_1 + I_2 = I_B 2 \quad \text{--- (2)}$$

$$\frac{0 - V_2}{R_i} + \frac{V_o I_o - V_2}{R_f} = \frac{V_2}{R_i} \quad \text{--- (3)}$$

$V_o I_o = 0$ / P offset Voltage due to i/p bias Current

$R_i =$ i/p Resistance

$$\frac{V_o I_o}{R_f} = V_2 \left[\frac{1}{R_i} + \frac{1}{R_f} + \frac{1}{R_i} \right] \quad \begin{matrix} \text{[Rearrangement of above]} \\ \text{Eq} \end{matrix} \quad \text{--- (4)}$$

$$\frac{V_o I_o}{R_f} = V_2 \frac{R_i + R_f}{R_i R_f} \quad \text{--- (5)}$$

Sub in Eq (5) the value of V_2 from Eq (4)

$$V_o I_o = R_i R_f I_B 2 \left[\frac{R_i + R_f}{R_i} \right]$$

$$V_o I_o = R_f I_B 2$$

$$V_o I_o = R_f I_B \quad \text{from Eq (2)}$$

To reduce O/P offset Voltage due to input bias Current I_B .


$$V_2 = R_f I_B 2$$

$$R_f = \frac{R_i R_f}{R_i + R_f}$$


Inverting Amps and Non-inverting Amps

Ideal


Inverting Amplifier :-

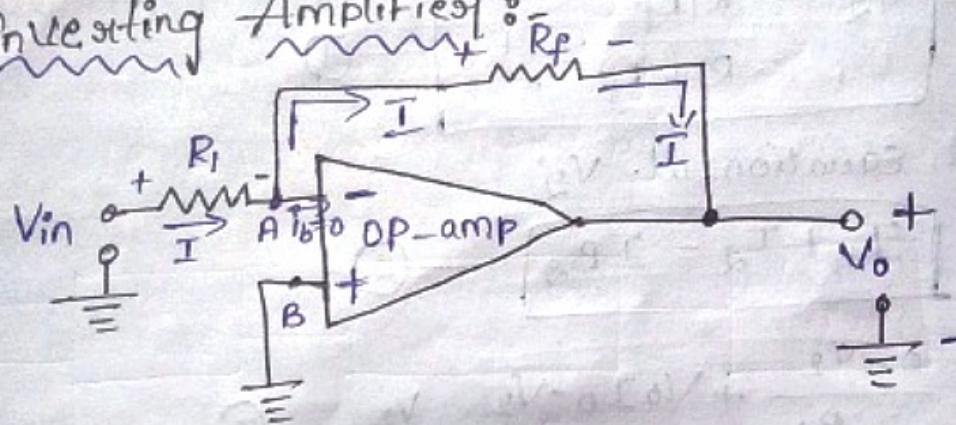

Operational Amplifier :-

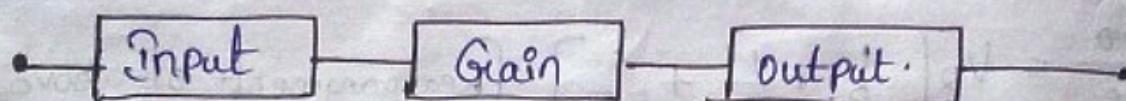

Circuit diagram :-

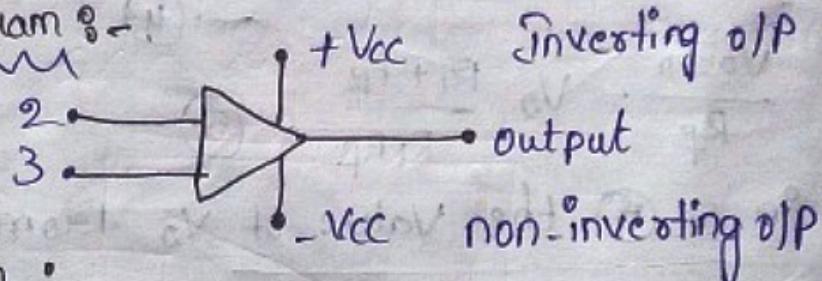

Pin diagram :-


offset	1	8	NC
Inverting terminal	2	7	+Vcc
non-inverting	3	6	O/P
-Vcc	4	5	offset

[Ideal op-Amplifier]


Ideal - operation - Amplifiers :- The ideal operation amplifiers identifies the differential b/w the two i/p signals applied at the inverting and non-inverting terminals and amplifies the different and produce an output Signals.

Equivalent Circuit of OP-Amp :-

Symbol:-

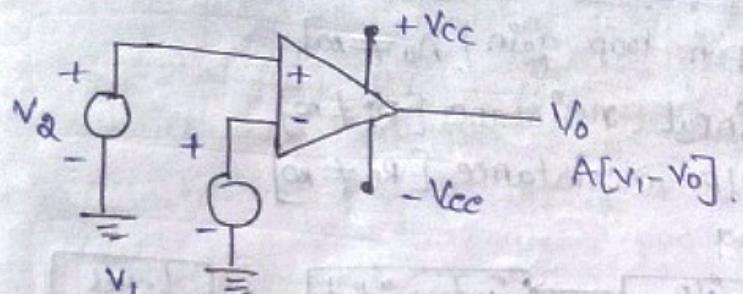

Transfer characteristics :-

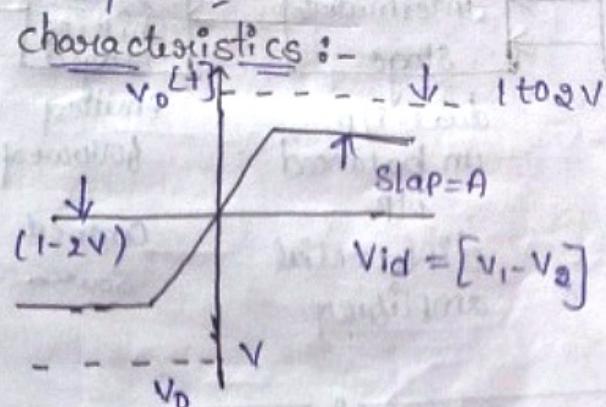

Differential op.

Ideal op-amp characteristics:-

Infinite Input Resistance [$R_i = \infty$]

Zero output resistance [$R_o = 0$]

Infinite Voltage gain [$A_v = \infty$]

Infinite Bandwidth [$BW = \infty$]

No common mode Rejection ratio [$CMRR = \infty$]

No Slew rate = ∞


Zero offset ; when [$V_1 = V_2$] [$V_o = 0$]

Characteristics do not shift with temperature.

Practical OP-amp :-

Inverting voltage

Inverting IP

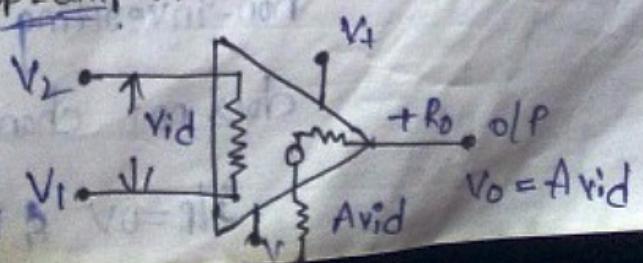


Characteristics of Practical Op-Amp :-

open loop gain [$A_O \neq \infty$]

input resistance [$R_i \neq \infty$]

Output resistance [$R_o \neq \infty$]

Inverting

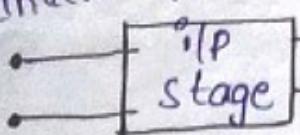

Intermediate stage

Level Shifting stage

Output stage

Non-inverting

dual IP
un balanced
OP

emitter
follower
current
source



complementary
system
Push-Pull
Amplifier

Dual IP
Balance of OP
differential
amplifiers

differential
amplifiers

Inverting Amplifier :- (ideal inverting Amplifier).

Ideal.

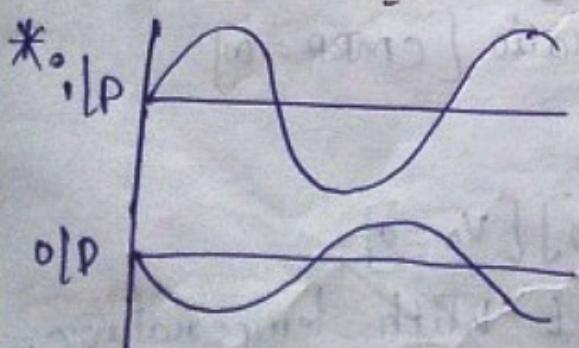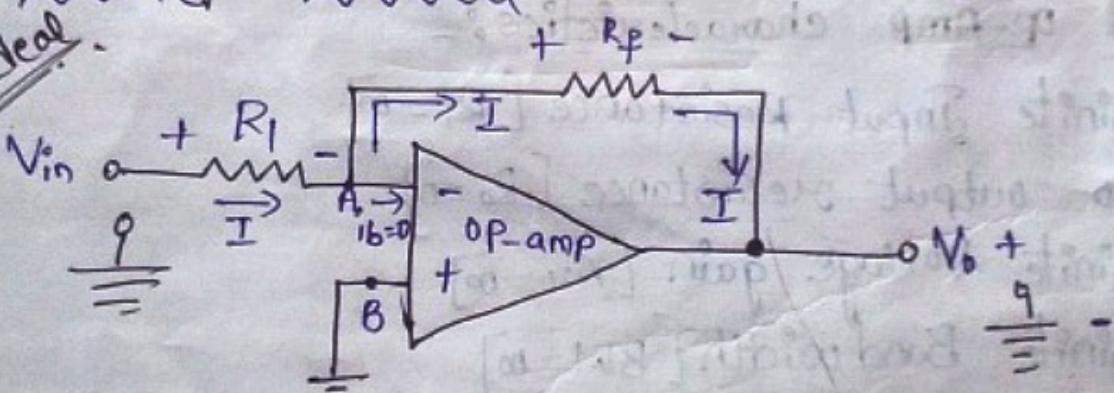


* The phase shift of the inverting Amplifier is 180° .

* The phase shift of the non-inverting Amplifier does not change

$$i_{IP} = 0V \quad \& \quad i_{OP} = 0V$$

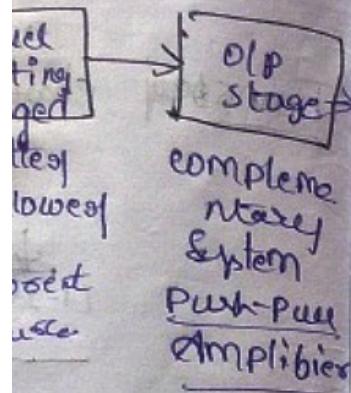- * An Amplifier is inverted as compare to the I/P Signal, the inverted O/P signal means having a phase shift of 180° compare to the I/P signal
- * The phase shift b/w I/P & O/P is 180° , such an amplifier is called inverting Amplifier.



Closed loop voltage gain :-

\rightarrow At node B is grounded, node A is also at ground potential of virtual ground

$$V_A = 0$$

The Current

$$I = \frac{V_{in} - V_A}{R_1}$$

$$I = \frac{V_{in}}{R_1} \quad | V_A = 0$$

I/P side :

O/P side :-


$$I = \frac{V_A + V_o}{R_F}$$

$$I = -\frac{V_o}{R_F} \quad | V_A = 0$$

Gain formula of
Inverting Amplifier.

$$A_{vf} = \frac{V_o}{V_{in}} = \frac{-R_F}{R_1}$$

Non-Inverting Amplifier :- (ideal).

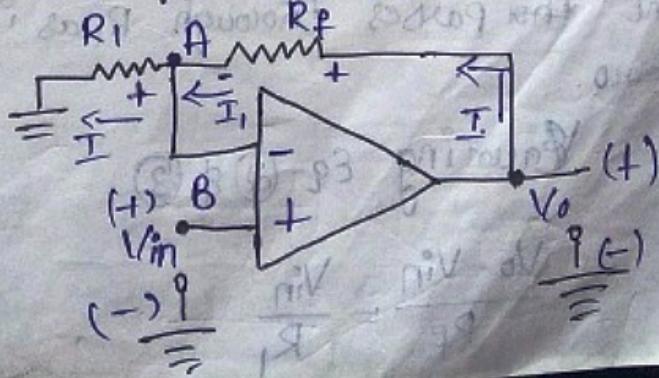

- * The amplifier which amplifies without producing any phase shift b/w input and output is called non-inverting Amplifier.
- * So the IP is applied to non-inverting terminal of op-amp.

Closed loop Gain :-

- * The node 'B' at potential V_B , the potential of point A, Same as 'B' which is V_{in} from the concept of virtual ground.

* Input Side :- $V_A = V_B = V_{in}$ — (1)

Output Side :- $I = \frac{V_o - V_A}{R_f}$

$$I = \frac{V_o - V_{in}}{R_f} \quad (2)$$

At the inverting terminal:

$$I = \frac{V_A - 0}{R_i}$$

$$I = \frac{V_A}{R_i} = \frac{V_{in}}{R_i}$$

$$I = \frac{V_{in}}{R_i} \quad (3)$$

Entire Current that passes through R_i as IP current is 3rd.

(1) Equating Eq (2) & (3)

$$\frac{V_o - V_{in}}{R_f} = \frac{V_{in}}{R_i}$$

without
it and output
testing terminal

Potential of
from the

$$\frac{V_o}{R_f} = \frac{V_{in}}{R_f} + \frac{V_{in}}{R_i}$$

$$\frac{V_o}{R_f} = V_{in} \left[\frac{R_i + R_f}{R_i R_f} \right]$$

$$\frac{V_o}{V_{in}} = \frac{R_i + R_f \times R_p}{R_i R_p}$$


$$\boxed{\frac{V_o}{V_{in}} = \frac{R_i + R_f}{R_i}}$$

Gain of the non-inverting
terminal.

$$\boxed{A_{vfp} = \frac{V_o}{V_{in}} = 1 + \frac{R_f}{R_i}}$$

Practical :-

Practical Inverting Amplifiers :-

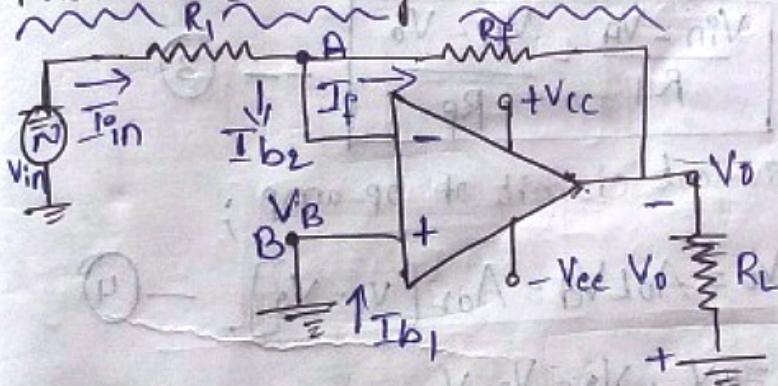

* Its I/p resistance "R_{in}" is less than (∞), so
op-amp I/P current is (∞).

* Open loop voltage Gain (A_{OL}) less than (∞).

* If, OLP resistance is "R_o" is not zero.

* System "R_f" forms feedback circuit, The Amplifier
inverted o/p voltage applied to inverting terminal
through feed back resistance "R_f". The o/p voltage
which is fed back opposite to the polarity of i/p

as i/p curr

Voltage.

* So the feedback said to be Negative.

Closed loop Voltage Gain:

* The closed loop voltage gain (A_{CL}) ratio of o/p voltage to i/p voltage with feedback.

* Applying KCL at node "A"

$$I_{in} = I_{ba} + I_f \quad \text{--- (1)}$$

$$I_{in} \approx I_f \quad (R_{in} \neq \infty)$$

I_{ba} is neglected

$$I_{in} \approx I_f \quad \text{--- (2)}$$

$$\frac{V_{in} - V_A}{R_1} = \frac{V_A - V_o}{R_f} \quad \text{--- (3)}$$

* from the equivalent circuit of op-amp;

$$V_o = A_{OL} V_d = A_{OL} [V_1 - V_2] \quad \text{--- (4)}$$

$$V_1 = 0V, V_2 = V_A$$


$$V_o = -A_{OL} V_A \quad \text{--- (5)}$$

Sub eq (5) in eq (3).

$$\frac{V_{in} + \frac{V_o}{A_{OL}}}{R_1} = \frac{-V_o}{A_{OL}} - \frac{V_o}{R_f}$$

$$= \frac{-A_{OL} V_A}{R_1 - V_o / R_f}$$

Practical

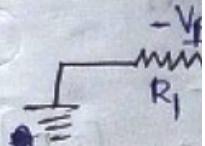

* The input op-amp, so input voltage where V_f is the input voltage, the closed loop gain is A_{CL} .

Ratio of
dback.

8/8/2023

$$V_{in} R_f + \frac{V_o}{AOL} = -\frac{R_i}{AOL} V_o - R_i V_o$$

$$V_{in} R_f = -V_o \frac{R_i}{AOL} + R_i + \frac{R_f}{AOL}$$

$$AOL = \frac{V_o}{V_{in}}$$

$$AOL = \frac{AOL R_f}{R_i + R_f + R_i AOL}$$

$$AOL = \frac{AOL R_f}{R_i + R_f + R_i AOL}$$


$$= -\frac{AOL V_A}{-V_o \left[\frac{R_i}{AOL} + R_f + \frac{R_f}{AOL} \right]}$$

$$V_{in} R_f = -V_o \left[\frac{R_i + R_i AOL + R_f}{AOL} \right]$$

$$= \frac{V_A}{-V_o \left[\frac{R_i}{AOL} + R_f \right]}$$

$$V_{in} = -V_o \left[\frac{R_i + R_i AOL + R_f}{AOL \cdot R_f} \right]$$

Practical Non-inverting Amplifier :-

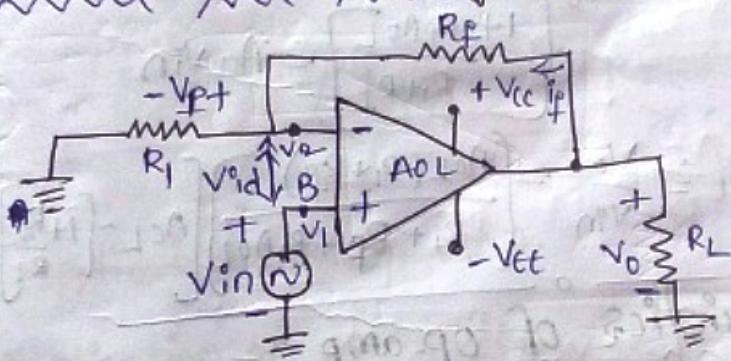

* The input is given at the non-inverting input of the op-amp, so op-amp always amplifies the difference input voltage V_d . The difference b/w the voltages V_{in} & V_f where V_f is feedback voltage opposes the input to voltage, that is 180° out of phase with respect to the input.

Closed-loop voltage gain :-

$$AOL = \frac{V_o}{V_{in}} \quad (1)$$

$$V_o = A_{OL} V_d \quad \text{--- ①}$$

$$V_o = A_{OL}(V_1 - V_2) \quad \text{--- ②}$$

$V_1 = V_{in}$ as op-amp applied

$V_2 = V_f$ voltage across R_f

Using voltage divider rule

$$V_f = \frac{V_o}{R_f} R_i \text{ as } R_{in} \rightarrow R_i$$

Substituting in eq ②

$$V_o = A_{OL} \left[V_{in} - \frac{R_f V_o}{R_i + R_f} \right]$$

$$V_o = A_{OL} V_{in} - \frac{R_f A_{OL} V_o}{R_i + R_f}$$

$$\frac{V_o}{V_{in}} \left[1 + \frac{R_f A_{OL}}{R_i + R_f} \right] = A_{OL} V_{in}$$

$$A_{OL} = \frac{V_o}{V_{in}} = \left[\frac{A_{OL} (R_i + R_f)}{R_i + R_f + R_i A_{OL}} \right] \left[A_{OL} - \left(1 + \frac{R_f}{R_i} \right) id \right]$$

DC characteristics of op-amp :-

- 1) input bias current
- 2) input offset current
- 3) input offset voltage
- 4) Thermal drift.

Thermal drift :-

The op-amp parameters i.e. offset Voltage (V_{ios})

input bias current (I_b) and input offset current

(I_{ios}) are not constant, varying with the factors

one) temperature (two) Supply Voltage, change (3) time.

Ac characteristic of op-amp :-

- 1) slew rate
- 2) frequency Response.

Power of Supply Rejection Ratio :- (PSRR)

It is defined as ratio of change in offset voltage due to change in supply voltage producing it keeping other power supply voltage constant. It is also called power supply sensitivity.

$$PSRR = \frac{\Delta V_{ios}}{\Delta V_{ee} / V_{cc} - \text{constant}}$$

Unit - II

Application of Op-amp :-

Application of op-amp :-

1) Summation (or) Adder Circuit :-

Inverting Summer :-

